 


One-Hot Encoded Finite State Machines

Example State Machine




State A = 00
 State B = 01
 State C = 10
 State D = 11

InA	InB	CS	NS	Z
0	-	A	A	0
1	-	A	B	0
0	-	B	A	1
1	-	B	C	1
-	0	C	C	1
-	1	C	D	1
-	-	D	A	0



InA	InB	CS	NS	Z
0	-	00	00	0
1	-	00	01	0
0	-	01	00	1
1	-	01	10	1
-	0	10	10	1
-	1	10	11	1
-	-	11	00	0


Example Machine Implementation

 

$$N1 = Q1 \cdot Q0' + Q1' \cdot Q0 \cdot \text{InA}$$


$$N0 = Q1 \cdot Q0' \cdot \text{InB} + Q1' \cdot Q0' \cdot \text{InA}$$

$$Z = Q1' \cdot Q0 + Q1 \cdot Q0'$$

 

Logic Used:

 - 9 gates
- 21 gate inputs
- 2 flip flops



Choose a Different Encoding

- A=1000, B=0100, C=0010, D=0001

InA	InB	CS	NS	Z
0	-	1000	1000	0
1	-	1000	0100	0
0	-	0100	1000	1
1	-	0100	0010	1
-	0	0010	0010	1
-	1	0010	0001	1
-	-	0001	1000	0

This is called a *one-hot* encoding.

Only one state bit is on at a time

InA	InB	CS	NS	Z
0	-	1---	1000	0
1	-	1---	0100	0
0	-	-1--	1000	1
1	-	-1--	0010	1
-	0	--1-	0010	1
-	1	--1-	0001	1
-	-	---1	1000	0

Because of the state encodings, there are many illegal states.

This TT with all these input don't cares is the result

One-Hot Encoding Results

- Will require 4 flip flops
 - One per state
 - Call the current state bits A, B, C, and D
 - Call the next state bits NA, NB, NC, and ND

By inspection we see:


$$NA = A \cdot \text{InA}' + B \cdot \text{InA}' + D$$

$$NB = A \cdot \text{InA}$$






$$NC = B \cdot \text{InA} + C \cdot \text{InB}'$$

$$ND = C \cdot \text{InB}$$

$$Z = B + C$$

 

One-Hot Implementation

     


Logic Used:

- 9 gates
- 19 gate inputs
- 4 flip flops

One-Hot Observations

- Choosing a one-hot encoding results in many, many don't cares in transition table
- Minimization results in simpler IFL and OFL
- Requires more flip flops
- Can do one-hot design by inspection
 - *Without using transition tables...*


Another One-Hot Example

 

State	Encoding
A	100
B	010
C	001

State Encoding and Structure

State	Encoding
A	100
B	010
C	001

 


With one-hot encoding, each state has its own flip flop.

'A' is the name of a state *and* it is the name of the wire coming out of the flip flop for state 'A'.

The same holds true for states 'B' and 'C'

One-Hot Encodings By Inspection

 


When is A the next state?

Look at the arcs entering state A

$$N_A = \mathbf{A \bullet x'} + B \bullet y'z + C$$

One-Hot Encodings By Inspection

 


When is A the next state?

Look at the arcs entering state A

$$N_A = A \bullet x' + \mathbf{B \bullet y'z} + C$$

One-Hot Encodings By Inspection

 


When is A the next state?

Look at the arcs entering state A

$$NA = A \bullet x' + B \bullet y'z + \textcolor{red}{C}$$

One-Hot Encodings By Inspection

 

When is A the next state?

Look at the arcs entering state A


$$N_A = A \bullet x' + B \bullet y'z + C$$

Similar reasoning leads to:

$$N_B = A \bullet x + B \bullet y'z'$$

$$N_C = B \bullet y$$


The Key Lock Problem - One-Hot Version

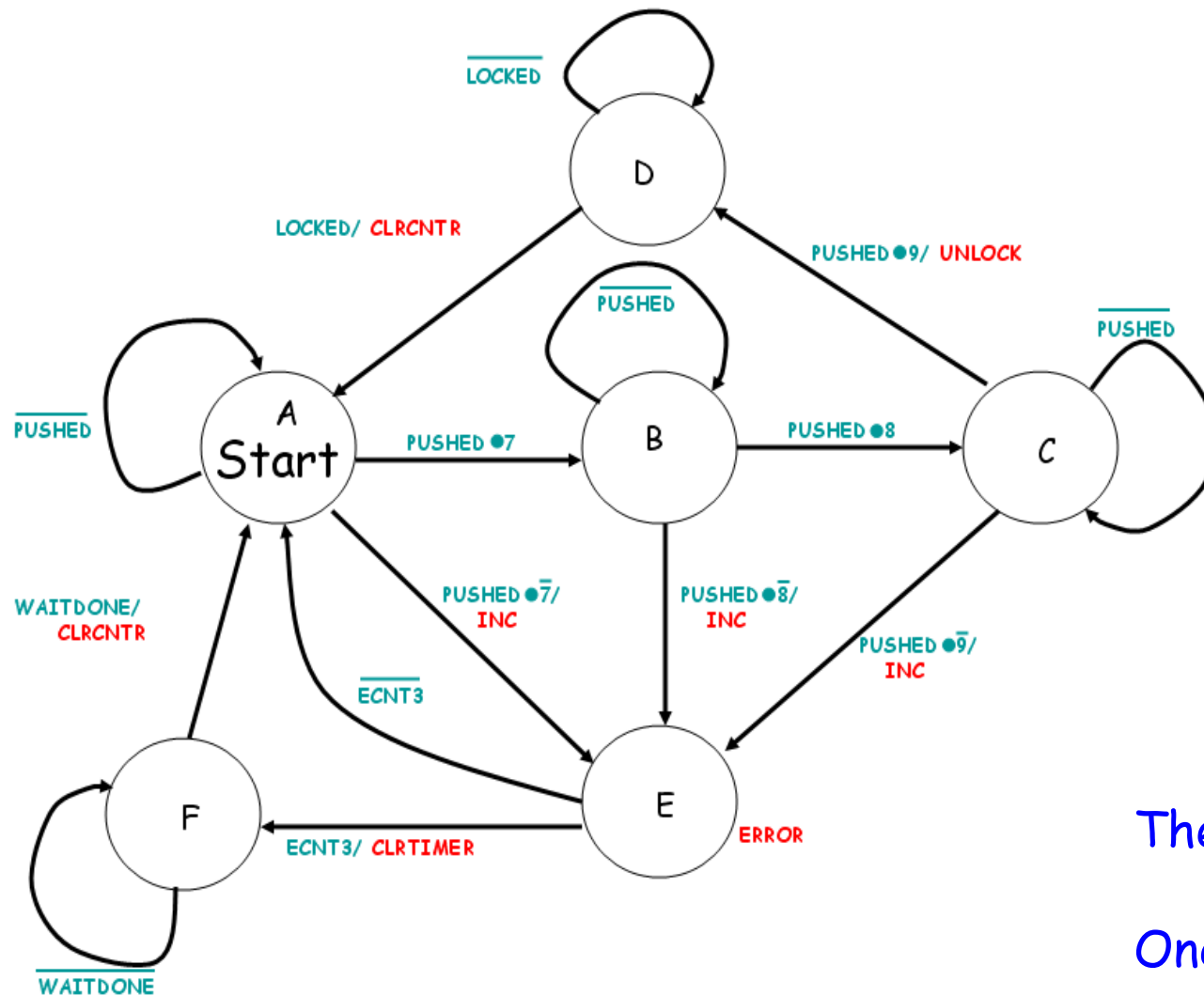

There will be 6 flip flops

One for each state

Key Lock Input Forming Logic

 

$$NA = (\text{PUSHED}' \cdot A) + (\text{ECNT3}' \cdot E) \\ + (\text{WAITDONE} \cdot F) \\ + (\text{LOCKED} \cdot D)$$

$$NB = (\text{PUSHED}' \cdot B) + (\text{PUSHED} \cdot 7 \cdot A)$$


$$NC = (\text{PUSHED}' \cdot C) + (\text{PUSHED} \cdot 8 \cdot B)$$

$$ND = (\text{LOCKED}' \cdot D) + (\text{PUSHED} \cdot 9 \cdot C)$$

$$NE = (\text{PUSHED} \cdot 7' \cdot A) \\ + (\text{PUSHED} \cdot 8' \cdot B) \\ + (\text{PUSHED} \cdot 9' \cdot C)$$


$$NF = (\text{ECNT3} \cdot E) \\ + (\text{WAITDONE}' \cdot F)$$

Key Lock Output Forming Logic

 


ERROR =

Key Lock Output Forming Logic

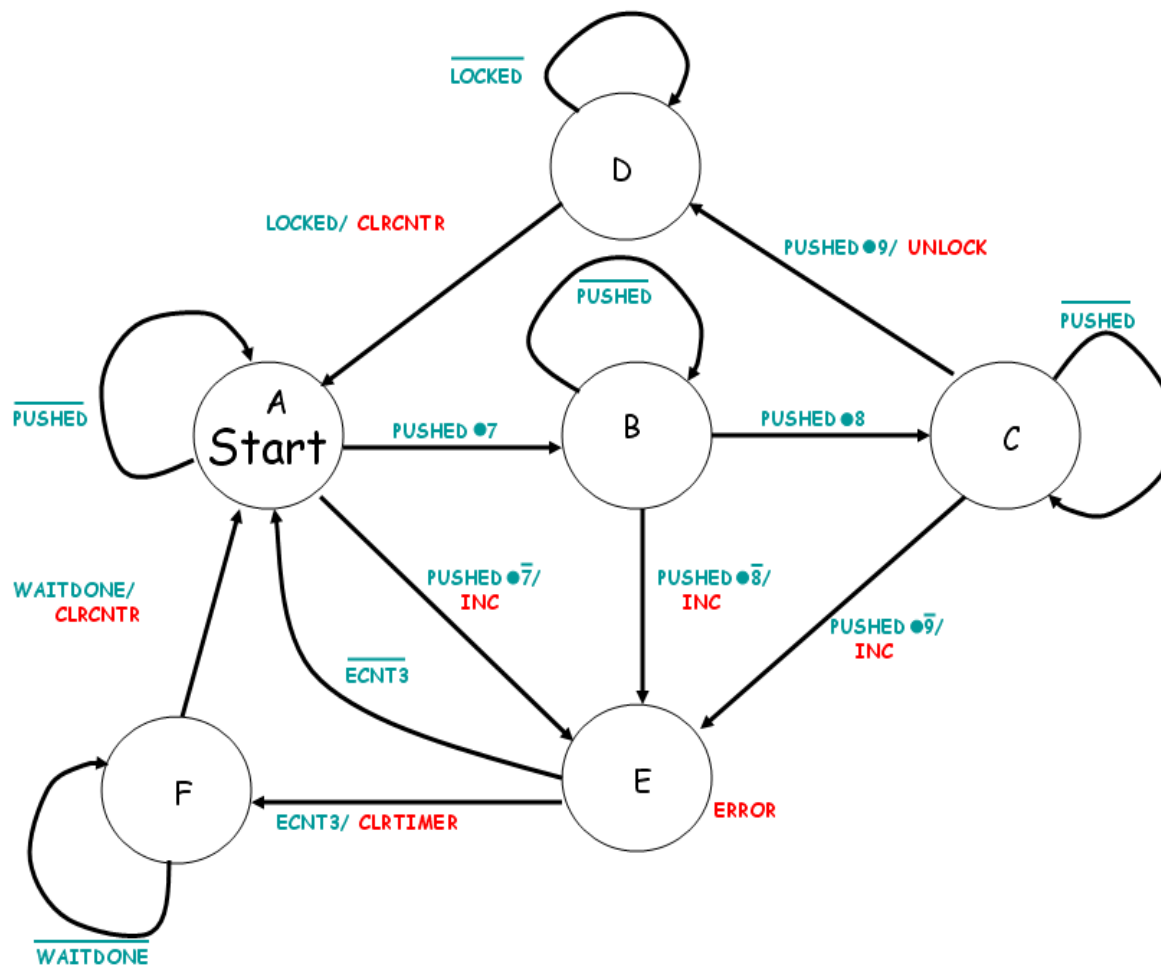


ERROR = E
INC =

Key Lock Output Forming Logic

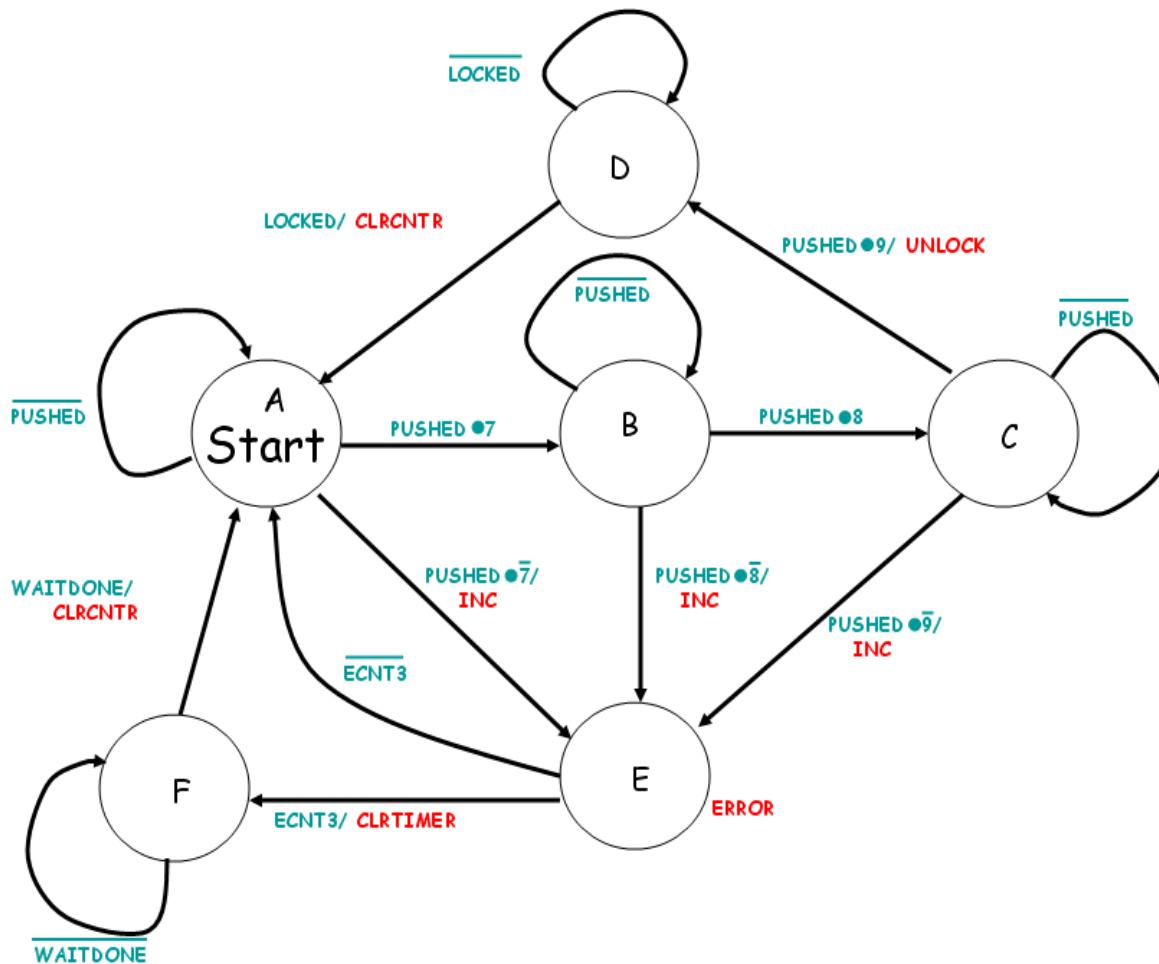


$ERROR = E$
 $INC = (PUSHED \cdot 7' \cdot A)$
 $\quad + (PUSHED \cdot 8' \cdot B)$
 $\quad + (PUSHED \cdot 9' \cdot C)$
 $CLRTIMER =$

Key Lock Output Forming Logic

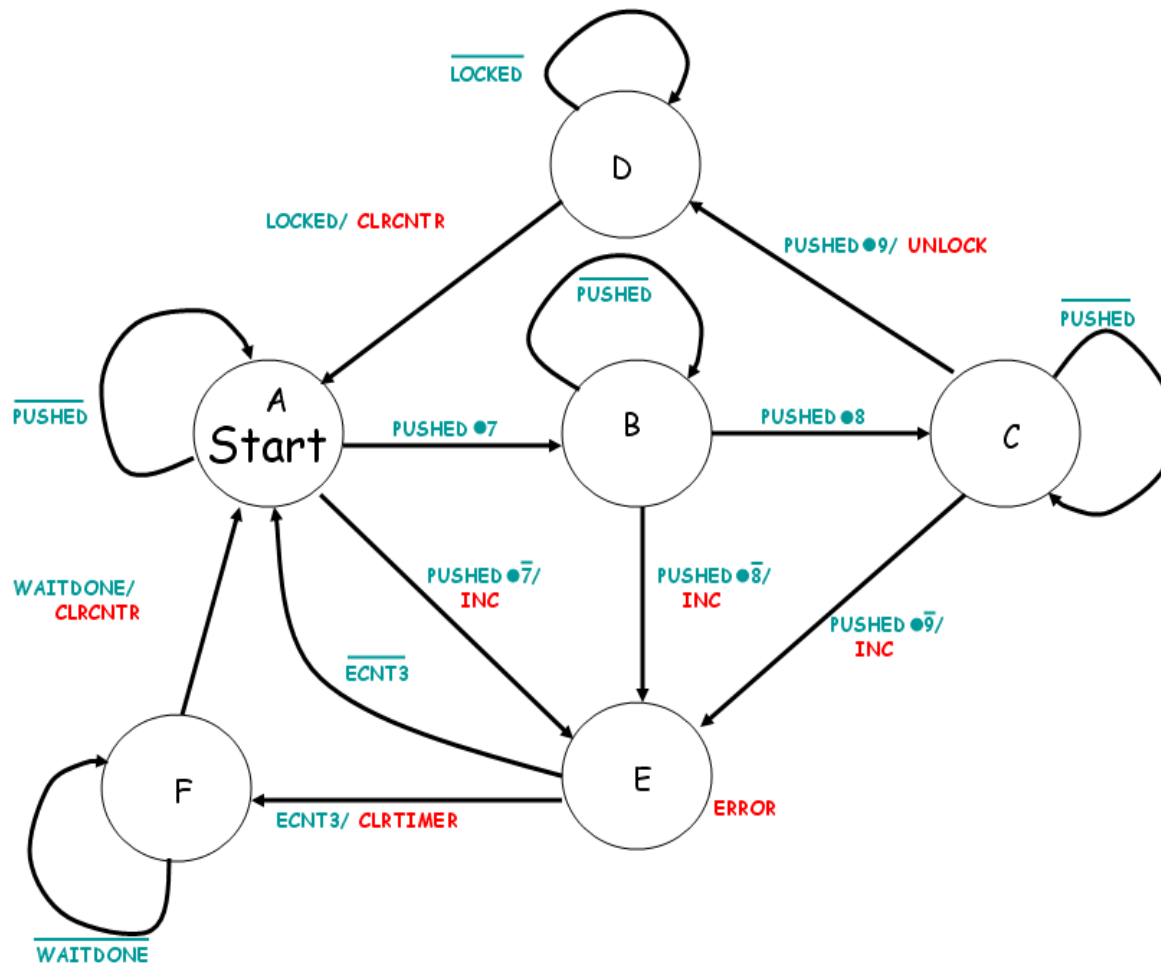

$ERROR = E$
 $INC = (PUSHED \cdot 7' \cdot A)$
 $\quad + (PUSHED \cdot 8' \cdot B)$
 $\quad + (PUSHED \cdot 9' \cdot C)$
 $CLRTIMER = ECNT3 \cdot E$
 $CLRCNTR =$

Key Lock Output Forming Logic

 

ERROR = E


INC = (PUSHED·7'·A)
+ (PUSHED·8'·B)
+ (PUSHED·9'·C)

CLRTIMER = ECNT3·E

CLRCNTR = (WAITDONE·F)
+ (LOCKED·D)

UNLOCK =

Key Lock Output Forming Logic

 

$ERROR = E$
 $INC = (PUSHED \cdot 7' \cdot A)$
 $\quad + (PUSHED \cdot 8' \cdot B)$
 $\quad + (PUSHED \cdot 9' \cdot C)$
 $CLRTIMER = ECNT3 \cdot E$
 $CLRCNTR = (WAITDONE \cdot F)$
 $\quad + (LOCKED \cdot D)$
 $UNLOCK = (PUSHED \cdot 9 \cdot C)$

Other State Encoding Techniques

- You have learned the 2 extremes
 - Fully encoded (8 states \Leftrightarrow 3 state bits)
 - One-hot encoded (8 states \Leftrightarrow 8 state bits)
- A range of options exist in between
- A good choice of encoding
 - Can minimize IFL and OFL complexity
 - Algorithms have been developed for this...
 - Beyond the scope of this class